



V/SEM/E & TC/2019 (S) [27-05-19, BACK]

POWER ELECTRONICS AND INDUSTRIAL CONTROL

Sub Code – ETT-501

Full Marks: 70

Time: 3 hours

Answer any **FIVE** Questions

The figures in the right-hand margin indicate marks

1. (a) Define latching current and holding current. 2
(b) Explain the principle of operation of SCR with V-I characteristics of Thyristor. 5
(c) Explain the turn on methods of thyristor. 7
2. (a) Write down the types of protections of thyristor. 2
(b) Explain the operation of UJT Relaxation oscillator with a neat diagram. 5
(c) Explain gate triggering of SCR using UJT oscillator circuit. 7
3. (a) State the main functions of free-wheeling diode and why it is needed. 2
(b) Explain the operation of single phase half wave controlled rectifier with RL load and give its output diagram. 5
(c) Describe briefly about the snubber circuit and its essential. 7
4. (a) Classify the inverter according to the nature of input source. 2
(b) Explain the operation of single phase half bridge voltage source inverter with resistive load. 5
(c) Explain principle of step down and step up chopper operation. 7
5. (a) Classify choppers according to the directions of output voltage and current. 2
(b) Explain briefly about the constant frequency operation under the time ratio control strategy of chopper. 5
(c) Explain the operation of type A chopper. 7
6. (a) Describe cyclo-converter. 2
(b) Explain the basic structure of IGBT. 5
(c) Explain the operation of cyclo-converter with purely resistive load. 7
7. (a) Classify the power semiconductor devices and give two examples from each. 2
(b) Explain about the operation of buck converter. 5
(c) Explain briefly about the principle of online UPS. 7



V/SEM/E & TC/2018 (W) [DEC, REG]

POWER ELECTRONICS AND INDUSTRIAL CONTROL

Sub Code – ETT-501

Full Marks: 70

Time: 3 hours

Answer any FIVE Questions

The figures in the right-hand margin indicate marks

1. (a) List applications of SCR. [2]
(b) Explain the operation, construction of Power MOSFET & draw its characteristics curve. [5]
(c) Explain the operation, construction of IGBT and draw its characteristics curve. [7]
2. (a) State different methods of TURN ON of an SCR. [2]
(b) Explain the Auxiliary voltage commutations with neat circuit diagram and waveforms. [5]
(c) Explain synchronous triggering (ramp triggering). [7]
3. (a) Define Phase Angle, Extinction Angle of Controlled Rectifier. [2]
(b) Explain the principle of phase control and define firing angle (alpha) & conduction angle (beta) with the help of schematic and waveforms of Half wave controlled rectifier. [5]
(c) Explain with schematic diagram and waveforms the operation of single phase fully controlled bridge converter with RL load. [7]
4. (a) State the application of Chopper. [2]
(b) Explain different types of chopper configuration (Class A, Class B, Class C, Class D and Class F) briefly. [5]
(c) Explain principle of operation of Step Up and Down Chopper (Buck Boost Converts) [7]
5. (a) Define Inverter and State its Classification. [2]
(b) Draw the schematic diagram of single phase full bridge inverter (without commutation circuit) and explain its operation. [5]
(c) Explain a single phase to single phase Cycloconverter (Step Up and Step Down) with pure Resistive load with diagram and explain its waveform. [7]
6. (a) Give specification and ratings of Thyristors. [2]
(b) Describe how SCR can be protected against over voltage and over current. [5]
(c) Define Snubber Circuit and Design Snubber Circuit. [7]
7. (a) Define online UPS system and offline UPS system. [2]
(b) Draw schematic diagram of SCR battery charger with neat circuit diagram and explain. [5]
(c) Draw a block diagram of UPS system and explain its operation and application. [7]



V/SEM/E & TC/2018 (S) [02-05-18, BACK]

POWER ELECTRONICS AND INDUSTRIAL CONTROL

Sub Code – ETT-501

Full Marks: 70

Time: 3 hours

Answer any FIVE Questions

The figures in the right-hand margin indicate marks

1. (a) Define Firing Angle and Extinction Angle of SCR. [2]
(b) With neat circuit diagram explain the working of Step-down Chopper. [5]
(c) Explain the construction, operation of SCR and draw its V-I characteristics curve. [7]
2. (a) Define Latching current and Holding current of SCR. [2]
(b) Draw the schematic diagram of a single phase half bridge voltage source inverter and explain Its operation. [5]
(c) With neat circuit diagram and waveforms explain briefly about RC-firing of SCR. [7]
3. (a) Differentiate between VSI and CSI. [2]
(b) Explain the construction, operation of GTO and draw its V-I characteristics curve. [5]
(c) With circuit diagram and waveforms explain the operation of fully controlled single phase Bridge converter with Resistive load. [7]
4. (a) What is a freewheeling diode and why it is needed? [2]
(b) With neat diagram explain the Auxiliary Voltage Commutation circuit of SCR. [5]
(c) Describe the working of different Chopper Configurations (Type A, B, C and D only) [7]
5. (a) What is Solid State Relay? [2]
(b) Draw burglar alarm circuit using SCR and explain its operation. [5]
(c) Explain the operation of a single phase full bridge inverter with neat circuit diagram. [7]
6. (a) Draw the circuit diagram of UJT as an SCR Triggering circuit. [2]
(b) Describe briefly different Turn ON Methods of SCR. [5]
(c) Draw and explain the operation of a single phase to single phase Step-Up Cycloconverter with pure resistive load. [7]
7. (a) Write the full forms of IGBT, SMPS, TRC and BTBF. [2]
(b) Explain Snubber circuit, draw circuit diagram for protections of SCR by Snubber circuit. [5]
(c) Explain the operation of ON LINE and OF LINE UPS with a neat circuit diagram. [7]

---ॐ--- ALL THE BEST ---ॐ--- ALL THE BEST ---ॐ---

Collected By:-

*Er. Paramananda Gouda
(Dept. of ETC, UCP Engg School)*



V/SEM/E & TC/2017 (W) [07-12-17, REG]

POWER ELECTRONICS AND INDUSTRIAL CONTROL

Sub Code – ETT-501

Full Marks: 70

Time: 3 hours

Answer any FIVE Questions

The figures in the right-hand margin indicate marks

1. (a) Write down the applications of power diode. [2]
(b) Explain Turn-ON & Turn-OFF behavior of power diode with current, voltage waveforms. [5]
(c) Explain construction, operation and V-I characteristics of a DIAC. Write down two applications of DIAC. [7]
2. (a) What are the different types of Power Transistor? [2]
(b) With neat diagram explain the two transistor analogy of SCR. [5]
(c) Explain the construction, operation and V-I characteristics of GTO. [7]
3. (a) What are the two general functions to be full filled by the gate control circuit? [2]
(b) Explain thermal triggering and radiation (light) triggering of an SCR. [5]
(c) What is commutation? What are the different types of commutation? Explain the line commutation circuit with waveforms. [7]
4. (a) What are firing angle (α), Conduction angle (γ) and Extinction angle (β)? [2]
(b) What is Integral Cycle Control (ICC)? [5]
(c) With neat circuit diagram and waveforms explain the operation of a single phase full-wave Controlled bridge convertor with resistive load. [7]
5. (a) What are the different types of choppers? [2]
(b) With neat circuit diagram and waveforms explain the operation of Buck-Boost Chopper. [5]
(c) With neat circuit diagram and waveforms explain the operation of Single Phase Full Bridge Voltage Source Inverter with Resistive Load. [7]
6. (a) Explain classification of cycloconverters. [2]
(b) What is duty cycle? Explain constant frequency method of controlling duty cycle of chopper. [5]
(c) With neat circuit diagram and waveforms explain the operation of single phase to single Phase cycloconverter with resistive load. [7]
7. (a) What are electrical failures in an SCR. [2]
(b) What is a Snubber circuit? Explain how it protects the SCR? [5]
(c) Give a comparative explanation of Linear Power Supply and Switched Mode Power Supply. Give some applications of SMPS. [7]



V/SEM/E & TC/2017 (S) [18-05-17, BACK]

POWER ELECTRONICS AND INDUSTRIAL CONTROL

Sub Code – ETT-501

Full Marks: 70

Time: 3 hours

Answer any FIVE Questions

The figures in the right-hand margin indicate marks

1.
 - a) Define holding current. [2]
 - b) Draw the four layer structure of SCR. [5]
 - c) Describe the different modes of operation of SCR. [7]
2.
 - a) Write any two application of TRIAC. [2]
 - b) Describe the working of a GTO. [5]
 - c) Describe the light triggering and temperature triggering methods of SCR. [7]
3.
 - a) What do you mean by commutation? [2]
 - b) Describe any one of the forced commutation technique with neat sketch. [5]
 - c) Describe how the Thyristor can be protected against overvoltage and over current. [7]
4.
 - a) Draw the symbols of SCR, GTO and Power MOSFET. [2]
 - b) Describe about the R-firing circuit. [5]
 - c) Describe the working of a simple phase controlled rectifier circuit. [7]
5.
 - a) What you mean by duty cycle? [2]
 - b) What is a chopper? Explain the operation of step down chopper. [5]
 - c) Explain the principle of operation of class-C chopper. [7]
6.
 - a) Define turn-on time of SCR. [2]
 - b) With necessary diagram describe the working of DIAC. [5]
 - c) Describe the operation of a Burglar alarm circuit. [7]
7.
 - a) What do you mean by firing angle? [2]
 - b) Describe SSR. Explain its operation with neat diagram. [5]
 - c) What is UPS? Explain the working of on-line and off-line UPS system. [7]

---------- ALL THE BEST ---------- ALL THE BEST ----------

Collected By:-

*Er. Paramananda Gouda
(Dept. of ETC, UCP Engg School)*



V/SEM/E & TC/2016 (W) [DEC, NEW]

POWER ELECTRONICS AND INDUSTRIAL CONTROL

Sub Code – ETT-501

Full Marks: 70

Time: 3 hours

Answer any **FIVE** Questions

The figures in the right-hand margin indicate marks

1.
 - a) Define firing angle and conduction angle of SCR. [2]
 - b) Explain the two transistor analogy of SCR. [5]
 - c) Explain the operation, construction of DIAC and draw the V-I characteristic. [7]
2.
 - a) Write down the application of IGBT. [2]
 - b) Explain the dynamic characteristic of SCR. [5]
 - c) Explain the operation, construction of IGBT and draw its V-I characteristic.
3.
 - a) Define commutation. [2]
 - b) What is firing circuit and draw and explain R-C firing circuit. [5]
 - c) Explain line commutation with circuit diagram and waveforms. [7]
4.
 - a) Define Chopper. [2]
 - b) Explain working fully controlled 1- Φ bridge converter of resistance load with waveforms.
 - c) Explain the operation of dual converter. [7]
5.
 - a) Define inverter and its applications. [2]
 - b) Explain the principle of operation of Buck-Boost converter. [5]
 - c) Draw the diagram of a single phase to single phase cycloconverter with pure resistive load & explain with neat waveforms. [7]
6.
 - a) Define Snubber circuit. [2]
 - b) Define on-line UPS system. Draw block diagram of UPS system & explain its operation.
 - c) Describe (dv/dt) and (di/dt) protection of SCR. [7]
7.
 - a) What is a freewheeling diode and why it is needed? [2]
 - b) Explain static circuit breaker. [5]
 - c) Draw schematic diagram of a single phase full bridge inverter & explain its operation. [7]

-----☪-----☪----- ALL THE BEST -----☪-----☪----- ALL THE BEST -----☪-----☪-----

Collected By:-

*Er. Paramananda Gouda
(Dept. of ETC, UCP Engg School)*



POWER ELECTRONICS AND INDUSTRIAL CONTROL

Sub Code – ETT-501

Full Marks: 70

Time: 3 hours

Answer any **FIVE** Questions

The figures in the right-hand margin indicate marks

1. (a) Draw the circuit symbol of power MOSFET and IGBT. [2]
(b) Explain the operation, construction of SCR and draw its V-I characteristics curve. [5]
(c) Explain the operation, construction of IGBT and draw its characteristics curve. [7]
2. (a) List applications of TRIAC (Phase control using TRIAC). [2]
(b) Draw UJT pulse trigger circuit and explain. [5]
(c) Explain the Auxiliary Voltage Commutation with circuit diagram. [7]
3. (a) Define firing angle (alpha) and Conduction angle (beat) of controlled rectifier. [2]
(b) Explain principle of operation of Step up and Step down chopper. [5]
(c) Explain with circuit diagram and waveforms of the operation of fully controlled single phase bridge converter with Resistive load. [7]
4. (a) Define inverter and its applications. [2]
(b) Draw the schematic diagram of single phase full bridge inverter (without commutation circuit) and explain its operation. [5]
(c) Draw the diagram of a single phase to single phase Cycloconverter (Step up and Step down) with pure Resistive load and explain and draw its waveform. [7]
5. (a) Define Cyclo converter and its applications. [2]
(b) Describe dv/dt and di/dt protection of SCR. [5]
(c) Design and explain Snubber Circuit and state its applications. [7]
6. (a) Define specification, ratings of Thyristor with example. [2]
(b) Draw a schematic diagram of SCR battery charger and explain. [5]
(c) Draw a block diagram of UPS system and explain its operation and applications. [7]
7. (a) Define only UPS system. [2]
(b) Draw diagram of AC voltage stabilizer and explain its operation. [5]
(c) Draw circuit diagram of Solid State Relay (SSR) and explain its operation [7]

---❧---❧---❧--- ALL THE BEST ---❧---❧---❧--- ALL THE BEST ---❧---❧---❧---

Collected By:-

*Er. Paramananda Gouda
(Dept. of ETC, UCP Engg School)*



V/SEM/E & TC/2015(W) DEC New

POWER ELECTRONICS AND INDUSTRIAL CONTROL

Sub Code – ETT-501

Full Marks: 70

Time: 3 hours

Answer any **FIVE** Questions

The figures in the right-hand margin indicate marks

1. (a) Draw V-I Characteristics of Power, Signal and Ideal Diode. [2]
(b) Discuss the two transistor model of a thyristor. Derive an expression for the anode current. [5]
(c) Explain the constructional details and working of low power MOSFET and bring out difference between low power MOSFET and High power MOSFET. [7]
2. (a) Define Holding Current and Latching Current. [2]
(b) Explain the operation, construction and application of Power Diode. [5]
(c) Enumerate various mechanisms by which thyristors can be triggered into conduction mode. Discuss these techniques which result in random turn on of a Thyristor? [7]
3. (a) What is Snubber circuit and why it is essential? [2]
(b) Define commutation and explain the working of impulse commutation method with neat circuit diagram and waveforms. [5]
(c) Explain different modes of operation, construction of TRIAC & draw its V-I characteristic. [7]
4. (a) Write down the application of phase controlled rectifiers. [2]
(b) With schematic diagram & waveforms, explain operation of 1ϕ semi converter with RL load. [5]
(c) Describe the working of a single phase full bridge inverter with its advantages. [7]
5. (a) State the difference between voltage source and current source inverter. [2]
(b) Explain the principle of operation of step up chopper. [5]
(c) Describe the working of a single phase parallel inverter with relevant circuit & waveforms [7]
6. (a) Define Time ratio control. [2]
(b) Explain the principle of operation of single phase to single phase step up Cycloconverter with pure resistive load with the help of bridge type configuration. [5]
(c) Describe the working of different Chopper Configurations (Type A, B, C and D only) [7]
7. (a) What are the advantages of freewheeling diode? [2]
(b) Draw a block diagram of UPS system and explain its operation and applications. [5]
(c) Write short notes on way **TWO**: [4×2=8]
 - (i) Buck Boost Converter
 - (ii) Switch mode power supply (SMPS)
 - (iii) GTO and its Applications.



POWER ELECTRONICS AND INDUSTRIAL CONTROL

(Sub Code: Theory - 1)

Full Marks: 80

Time: 3 hours

Answer any **FIVE** Questions

The figures in the right-hand margin indicate marks

1. (a) Define reliability of SCR and Mean Time Between Failure (MTBF). [2]
(b) Explain principle of operation of step-up chopper with resistive load and proper diagram and draw its waveform. [6]
(c) Explain the operation, construction of SCR and draw its V-I characteristics curve. [8]
2. (a) What is the basic difference between firing angle & extinction angle of controlled rectifier? [2]
(b) Define commutation and explain briefly about different TURN ON methods of SCR. [6]
(c) Explain briefly about R-C firing of SCR. [8]
3. (a) Differentiate between DIAC and TRIAC. [2]
(b) Discuss about the operation of power BJT. [6]
(c) Describe about different chopper configurations (class A, B, C & D,) with neat diagrams. [8]
4. (a) What are the disadvantages of Cycloconverter? [2]
(b) Draw the schematic diagram of linear power supply that provides +5V or -5V and explain its operation. [6]
(c) Explain the operation of single-phase full bridge inverter with schematic diagram. [7]
5. (a) What do you mean by duty cycle? [2]
(b) Explain the operation with diagram of a single phase to single phase Cycloconverter with resistive type load. [6]
(c) Explain the operation, construction of GTO and draw its characteristics curve. [8]
6. (a) Differentiate between ONLINE UPS and OFFLINE UPS system. [2]
(b) Explain the two transistor of SCR. [6]
(c) Draw schematic diagram of linear power supply that provides +15V or -5V using IC LM 317 and explain its operation. [8]
7. (a) What are the methods to protect a SCR? [2]
(b) Explain with schematic diagram and waveform the operation of a single phase fully controlled bridge converter with resistive load. [6]
(c) Write short notes on way **TWO**: [4×2=8]
 - (i) Smoke detector circuit
 - (ii) Switch mode power supply (SMPS)
 - (iii) Snubber circuit
 - (iv) Uninterruptable power supply (UPS)

---❧---❧---❧--- ALL THE BEST ---❧---❧---❧--- ALL THE BEST ---❧---❧---❧---

Collected By:-

*Er. Paramananda Gouda
(Dept. of ETC, UCP Engg. School)*



POWER ELECTRONICS AND INDUSTRIAL CONTROL

(Sub Code: Theory - 1)

Full Marks: 80

Time: 3 hours

Answer any **FIVE** Questions

The figures in the right-hand margin indicate marks

1. (a) Define holding current and surge current rating. [2]
(b) Explain the two transistor analogy of SCR. [6]
(c) Explain the operation, construction of TRIAC and draw V-I characteristics curve. [8]
2. (a) What are the applications of GTO? [2]
(b) Explain the operation, construction and application of Power Diode. [6]
(c) Explain the operation, construction of IGBT and draw its characteristics curve. [8]
3. (a) Define Reverse Recovery Time of SCR. [2]
(b) Define commutation and explain the working of Resonant commutation method with a neat circuit briefly. [6]
(c) Explain the R-Firing, R-C firing and Ramp Triggering circuit briefly. [8]
4. (a) Define phase angle and Extinction angle. [2]
(b) Explain with schematic diagram and waveform the operation of a single phase fully controlled bridge converter with Resistive load. [6]
(c) Draw the schematic diagram of single phase half bridge voltage source inverter and explain its operation. [8]
5. (a) Define Time Ratio Control. [2]
(b) Explain the principle of operation of step-down chopper with R-L load with a neat circuit diagram and give its waveform. [6]
(c) Describe the different chopper configurations (Class A, B, C & D only) [8]
6. (a) What are the advantages of Cycloconverter? [2]
(b) Draw the diagram of a single phase to single phase Cycloconverter with pure Resistive load and explain. [6]
(c) Design the Snubber circuit and why it is required. [8]
7. (a) What are three failures of SCR? [2]
(b) Define reliability of SCR and mean time between Failures (MTBF). [6]
(c) Draw a block diagram of UPS system and explain its operation and application. [8]
8. (a) What are the advantages of Fly Wheel Diode? [2]
(b) Draw a schematic diagram of linear power supply that provides + or -15V and explain its operation. [6]
(c) Write short notes on way two: - [4×2=8]
 - (i) Burglar alarm circuit
 - (ii) Solid State Relay
 - (iii) Temperature control circuit
 - (iv) SCR battery charger circuit.



POWER ELECTRONICS AND INDUSTRIAL CONTROL

(Sub Code: Theory - 1)

Full Marks: 80

Time: 3 hours

Answer any **FIVE** Questions

The figures in the right-hand margin indicate marks

1. (a) Define Latching current and Holding current. [2]
(b) Explain operation, construction of power MOSFET & list of application of MOSFET. [6]
(c) Explain the operation, construction of TRIAC and draw its V-I characteristics curve. [8]
2. (a) How the GTO differs from a thyristor? [2]
(b) Define briefly different methods of TURN ON of an SCR. [6]
(c) Define commutation and explain the operation resonant commutation method with neat circuit diagram and draw its waveform. [8]
3. (a) Define Phase angle and Extinction angle. [2]
(b) Define snubber circuit and design the snubber circuit. [6]
(c) Describe the working principle of single phase full-wave controlled rectifier with R-load with a neat diagram and draw waveform. [8]
4. (a) Define chopper and name of the devices which are used for implementation of chopper switch. [2]
(b) Explain briefly control strategies of chopper. [6]
(c) Explain principle the operation of step up & down chopper with a neat circuit diagram. [8]
5. (a) What is inverter and where it is used? [2]
(b) Explain the working principle the operation of single-phase full bridge inverter with a neat circuit diagram. [6]
(c) Explain the operation of a single phase to single phase Cycloconverter with resistive type load and what are the disadvantages of Cycloconverter? [8]
6. (a) Define Mean Time Between Failure. [2]
(b) Describe briefly overvoltage and over current protection of SCR briefly. [6]
(c) Explain the operation and working of switched mode power supply (SMPS) with a neat block diagram. [8]
7. (a) Define solid state relay. [2]
(b) Explain the operation and working of smoke detector circuit with neat block diagram. [6]
(c) Draw a block diagram of UPS system and explain its operation and application. [8]

ALL THE BEST

ALL THE BEST

Collected By:-

*Er. Paramananda Gouda
(Dept. of ETC, VCP Engg School)*



POWER ELECTRONICS AND INDUSTRIAL CONTROL

(Sub Code: Theory - 1)

Full Marks: 80

Time: 3 hours

Answer any **FIVE** Questions Including Q No 1 and 2

The figures in the right-hand margin indicate marks

1. Answer any **TEN** Question : [2×10 = 20]
 - a) Define latching current and holding current.
 - b) What is trapped charges and why it is essential?
 - c) What is natural commutation and where it is used?
 - d) Define phase angle and extinction angle.
 - e) What is mean time between failures (MTBF)?
 - f) What is PWM control and why it is better than frequency modulation control in chopper?
 - g) What is inverter and where it is used?
 - h) What is SMPS and what are its advantages over voltage regulators?
 - i) Define reverse recovery time and gate recovery time.
 - j) What is chopper and where it is used?
2. Answer any **FIVE** Question : [6×5 = 30]
 - a) Draw the layer diagram of SCR & explain the operation, construction & application of it.
 - b) Explain the operation and construction of IGBT and its application.
 - c) Describe the general layout diagram of RC and UJT triggering firing circuit with neat circuit diagram.
 - d) Explain with schematic diagram and waveforms the operation of single phase fully controlled bridge converter with resistive load only.
 - e) Why snubber circuit is needed and design the snubber circuit with a neat circuit diagram both for DC and AC circuit.
 - f) Explain the operation of timer (ON AND OFF Daley) circuit using IC 555.
 - g) Draw the diagram of a single phase to single phase step-up Cycloconverter with Resistive load and explain its operation.
3. Explain the principle of operation of step down, step-up and step-down converter with a neat circuit diagram. [10]
4. Explain classification of inverter and explain the operation of single phase full bridge inverter (without communication circuit) with a help of neat and circuit diagram. [10]
5. Explain the operation of ON LINE and OF LINE UPS with a neat circuit diagram. [10]
6. (a) Draw the circuit diagram of Solid State Relay (SSR) and explain its operation. [5]
(b) Draw burglar alarm circuit using SCR and explain its operation. [5]
7. (a) Explain the operation, construction of GTO with a neat circuit diagram. [5]
(b) Explain the operation of +5 volt linear regulated power supply with the help of neat circuit diagram. [5]